

# Ultra-low Power Motion Detection using the MSP430F2013

Zack Albus


MSP430 Applications

## ABSTRACT

Motion detection using pyroelectric passive infrared, or PIR, sensor elements is a common method used for such applications. An implementation of such a system using the 16-bit Sigma-Delta ADC integrated into the MSP430F2013 in order to detect motion is presented in this application report.

## 1 Hardware Design

A system capable of detecting motion using a dual element PIR sensor is shown in Figure 1 using the MSP430F2013 microcontroller. Using the integrated 16-bit Sigma-Delta analog-to-digital converter and built-in front-end PGA (SD16\_A), the MSP430F2013 provides all the required elements for interfacing to the PIR sensor in a small footprint. With integrated analog and a 16MHz, 16-bit RISC CPU, the MSP430F2013 offer a great deal of processing performance in a small package and at a low cost.

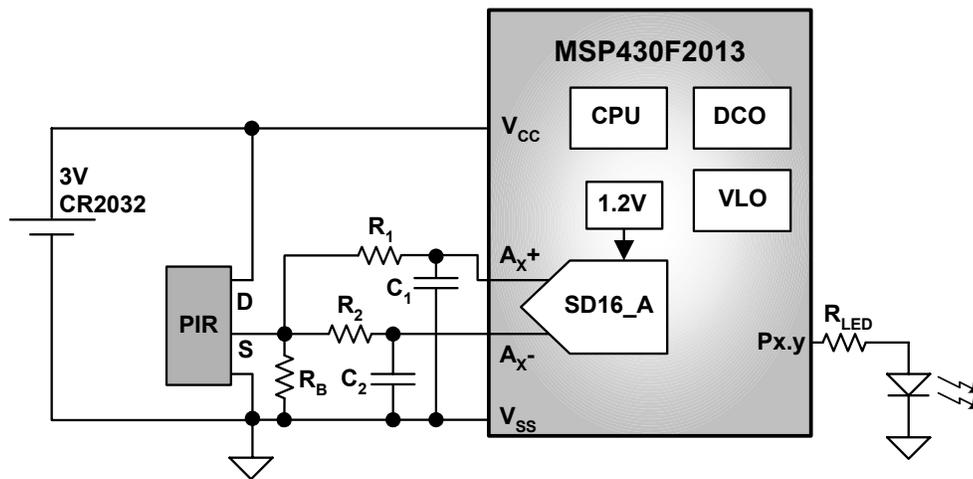


**Figure 1. MSP430F2013 Motion Detection System**

Figure 1 shows a simplified circuit that is used to process the PIR sensor output signal. The external components consist of the bias resistor,  $R_B$ , required for the sensor and two RC filters formed by  $R_1/C_1$  and  $R_2/C_2$ .

The two filters serve two different purposes. Since the input to the SD16\_A is differential, both a positive and negative input must be provided.  $R_1/C_1$  serves as an anti-aliasing filter on the  $A_{X+}$  input.

The second RC filter made up of  $R_2/C_2$  serves to create a DC bias for the  $A_{X-}$  input of the SD16\_A. This is required due to the large offset of the PIR source output with respect to  $V_{SS}$  with relation to the input range specification for the SD16\_A. Figure 2 below shows the respective signals in the circuit during detection of a motion event.

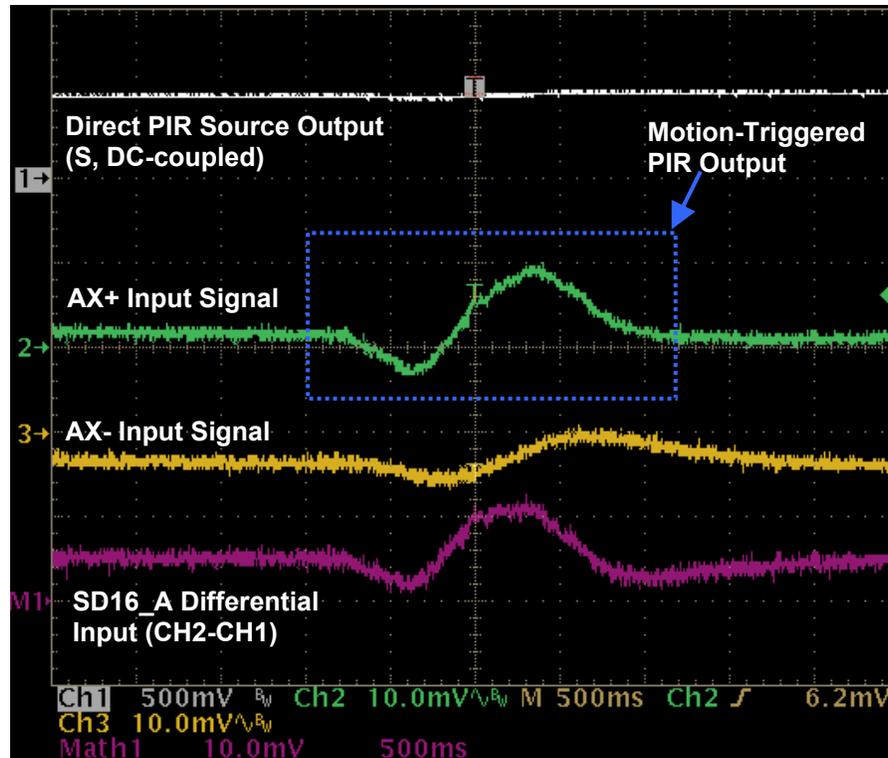

**Figure 2. PIR Sensor Output & Signal Conditioning**

In Figure 2, channel 1 is the direct output of the sensor. With a sensor drain voltage of 3V, the output offset is approximately 500mV. Connecting  $A_{X-}$  directly to  $V_{SS}$  and the sensor source output to  $A_{X+}$  would be valid only if the internal SD16\_A PGA gain setting is 1. With such a small peak-to-peak sensor output, as seen on channel 2, a higher gain setting is required eliminating the possibility that  $A_{X-}$  can be tied directly to  $V_{SS}$ .

Alternatively, a DC bias voltage can be generated to drive the  $A_{X-}$  input. This is created from the  $R_2/C_2$  low pass filter. This signal is shown on channel 3. The sensor output signal after the anti-aliasing filter connected to  $A_{X+}$  is shown on channel 2. By heavily low pass filtering the sensor output before connecting to  $A_{X-}$  as well, a simple DC bias is established, maintaining the input range requirements of the SD16\_A. The mathematical difference, CH2-CH3, is shown on M1. This is the differential voltage seen at the differential input pair,  $A_X$ , of the SD16\_A.

A PGA gain of 4x with an oversampling rate (OSR) of 256 has been used in this implementation. Additional gains and OSRs up to 32 and 1024, respectively, are possible for systems requiring additional sensitivity. Refer to the MSP430F2013 datasheet for possible SD16\_A PGA settings and appropriate analog input ranges.

In addition to the PIR sensor and the analog signal conditioning, a port pin is used to drive an LED. The LED is illuminated to indicate to the user that motion has been detected. This signal could also be used to drive an analog switch or relay to turn on a lamp or otherwise indicate motion in a real-world system.

As a final aspect of the hardware design, use of a Fresnel lens is critical to establishing good directionality of the sensor detection field. The internal architecture of the dual element sensor provides good noise immunity and false trigger rejection but also creates a limited directionality of the sensor's sensitivity. Use of the lens widens this field, making the final solution more robust.

## 2 Software Design

With low power as an essential goal in this application, analog sampling and data processing is kept to a minimum required to reliably detect motion. Figure 3 shows the software flow of the software implementation described.

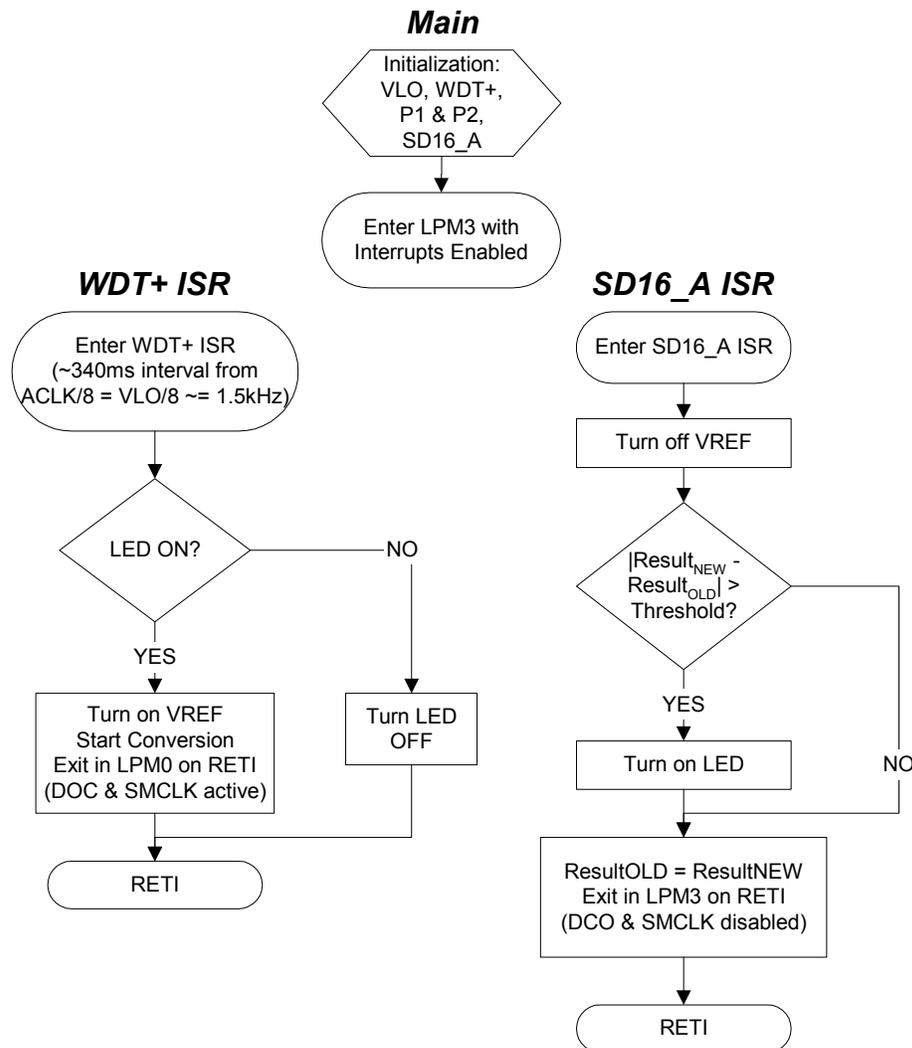


Figure 3. Motion Detection Software Flowchart

The software consists of three main elements: main routine, watchdog timer interrupt service routine and analog-to-digital converter interrupt service routine. The entire flow is interrupt driven using the internal very low frequency, very low power VLO oscillator. The VLO is approximately 12kHz and provided internally on the ACLK clock line. This signal is then divided by 8 and drives the WDT+ to give the CPU an interval wakeup of  $32768 \text{ clocks} / 12\text{kHz} / 8 = 341\text{msec}$ . After initialization of all peripherals the CPU enters into LPM3 via the VLO waiting for a WDT+ interrupt trigger.

After 341ms, the WDT+ ISR is entered and serves two basic functions: first, to start a new SD16\_A conversion and second, to control the LED indicating motion. In the case that no motion was detected in the last measurement (meaning the LED is off), the SD16\_A internal reference is enabled and a new conversion is started. Before exiting the WDT+ ISR, the status register value to be popped upon RETI is modified so that the DCO and SMCLK used to clock the SD16\_A will remain active. This causes the CPU to switch from LPM3 to LPM0 after RETI.

During this time, the SD16\_A is completing the conversion process. This takes  $256 \text{ clocks} / 1\text{MHz DCO} * 4 = 1.024\text{msec}$ . The factor of 4 comes from the INTDLYx setting of the SD16\_A. This setting allows the SD16\_A to take up to 4 conversions before interrupting the CPU to allow for any potential analog input changes that might impact the SD16\_A decimation filter, causing an invalid result. This is important since the SD16\_A is used in a single conversion mode in this application. Please refer to the MSP430x2xx Family Users Guide for more information concerning this setting.

After the conversion is complete, the SD16\_A ISR is entered and the internal reference is disabled. The absolute difference between the new result and the prior result is calculated, and compared against a preset threshold. When this threshold is exceeded, motion has been detected and the LED is enabled. The CPU exits the ISR back into LPM3 (DCO and SMCLK are disabled) and the next WDT+ interrupt is awaited.

### 3 Summary

Using this flow the average current consumption is maintained at a low level, low enough that the entire system can be powered from a standard CR2032 3V battery at approximately 9.4uA average  $I_{CC}$ . Table 1 shows the breakdown of operation versus current consumption.

**Table 1. Typical System Power Budget (over 1 second)**

Function	Duration	Active Current	Average Current
PIR325 sensor	1sec	6uA	6uA
SD16_A & VREF + DCO	1.024msec, ~2.94 times per sec	810uA+85uA	2.69uA
CPU Active (1MHz@3V)	262 MCLKs per sec: 262us	300uA	0.08uA
MSP430 Standby (LPM3 w/ VLO)	996.7msec	0.6uA	0.598uA
Total			<b>9.37uA</b>

The method shown here is quite simple in terms of the measurement and algorithm applied to detect motion. With up to 2K Flash and up to 16MIPs of processing power, the MSP430F2013 can be used to implement a much higher level of signal processing to add sensitivity as well as selectivity to a given PIR profile. The integrated analog and processing power of the MSP430F2013 family provides a low cost yet powerful MCU solution which can be used to differentiate custom motion detection applications.

#### **4 References**

1. MSP430x2xx Family User's Guide (SLAU144)
2. MSP430F20xx Mixed Signal Microcontroller Datasheet (SLAS491)
3. "Infrared Parts Manual: PIR325 & FL65", GLOLAB Corporation, [www.globlab.com](http://www.globlab.com), 2003

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

<b>Products</b>		<b>Applications</b>	
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>	Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>	Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>	Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>	Digital Control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>	Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>	Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>	Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
		Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
		Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
		Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

Mailing Address: Texas Instruments  
Post Office Box 655303 Dallas, Texas 75265